





Digital Logic Design

Hajar Falahati

**Department of Computer Engineering
IRAN University of Science and Technology**

hfalahati@iust.ac.ir

Memory Unit

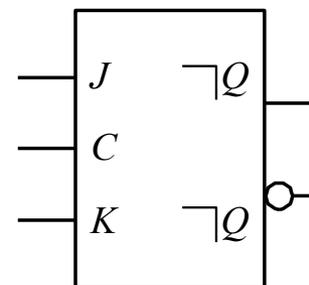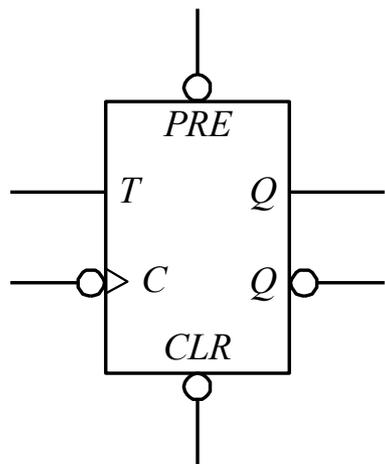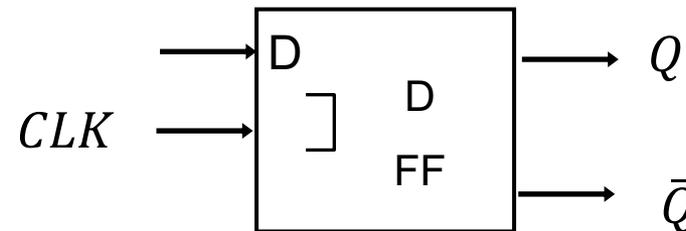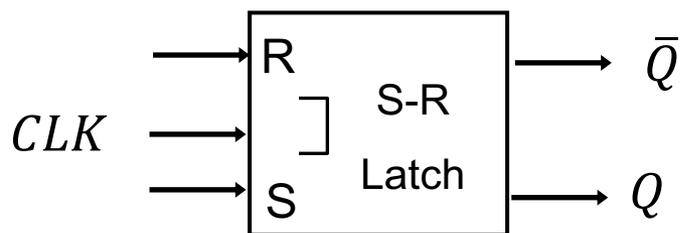

Outline


- Sequential Logics
 - Types
- Sequential Modules
 - Register
 - Counter



Modular Sequential Logics


Sequential Logics

- Types
 - Synchronous
 - Asynchronous

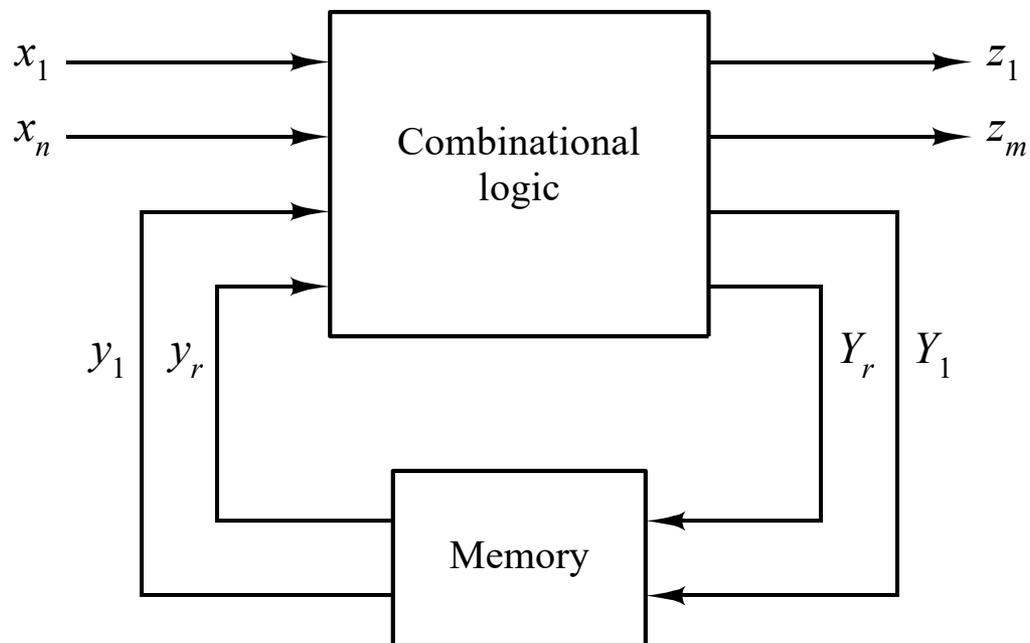


Synchronous Sequential Logics

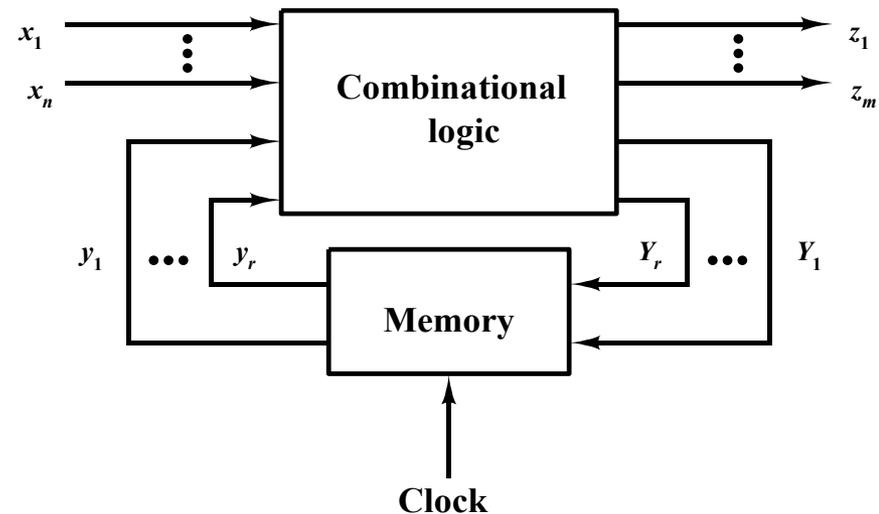- Circuit **behaves at discrete instance of time**
 - Determined by **CLK** signal
- **Storage** works only with the arrival of a clock pulse
- **CLK**
 - Avoids **instability** of the output
 - Clock Frequency = $1 / \text{clock cycle time}$
 - Cycles per second, Hz



Asynchronous Sequential Logics

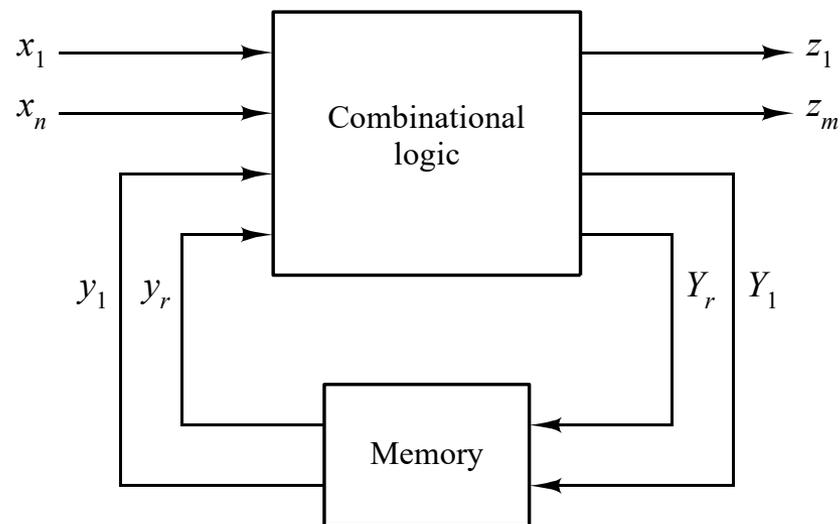- Circuit **behaves** based on input changes
- Circuit **behaves** at any instant of time
 - Output may **not** be stable
- Not common



Sequential Modules

- Register
- Shift Register
- Counter


Register

Register



- A collection of binary storage elements
 - Store a vector of binary values
 - Perform simple data storage
 - Perform data movement

Register: Sample 1

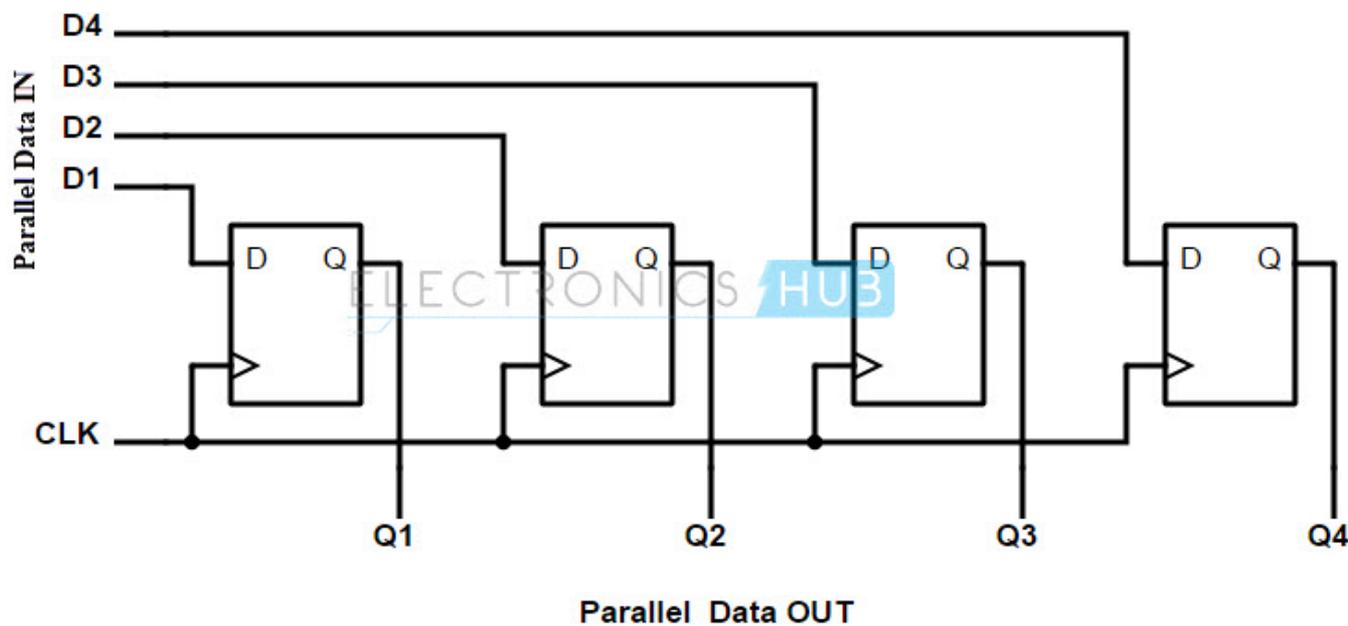- Synchronous register
- A collection of D FF




Register: Sample 1 (cont'd)

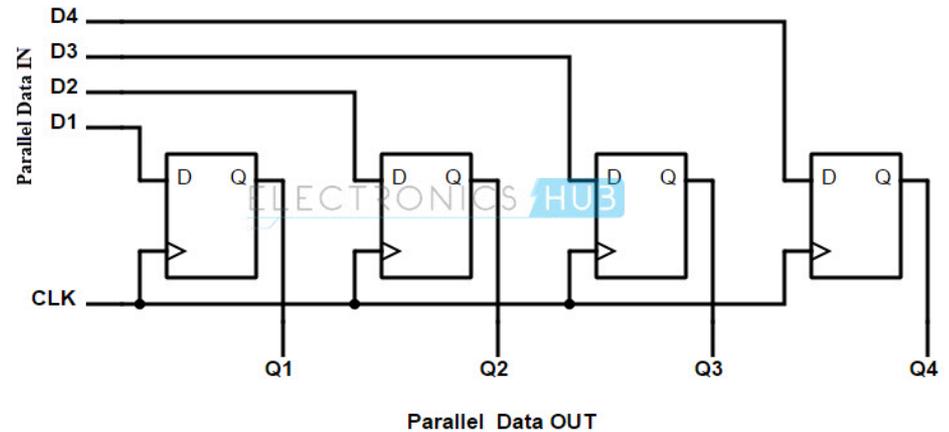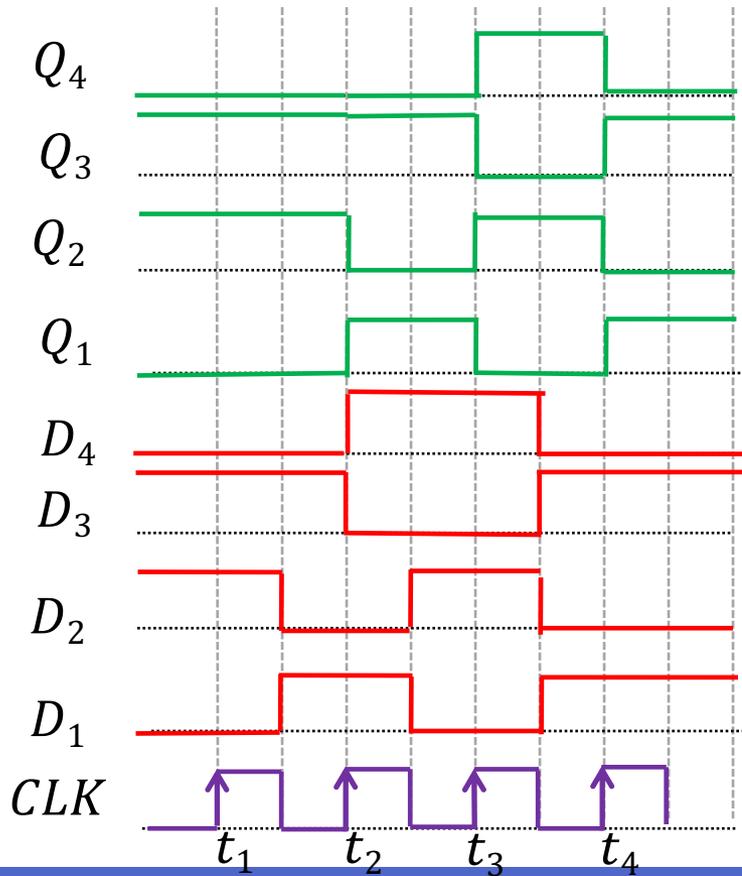

Register: Sample 1


- Register with **parallel load**

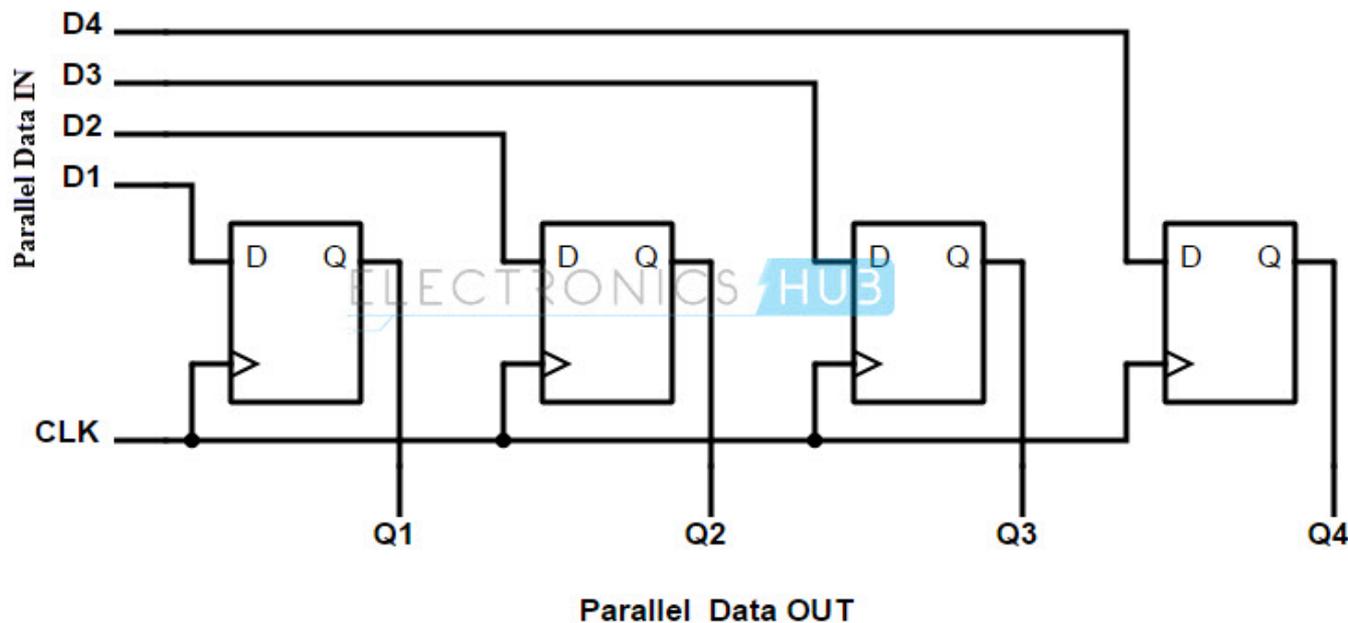

Register with Parallel Load


- Load (LD)
 - Control loading the new data to the register

<i>Load</i>	$Q(t + 1)$
0	$Q(t)$
1	D

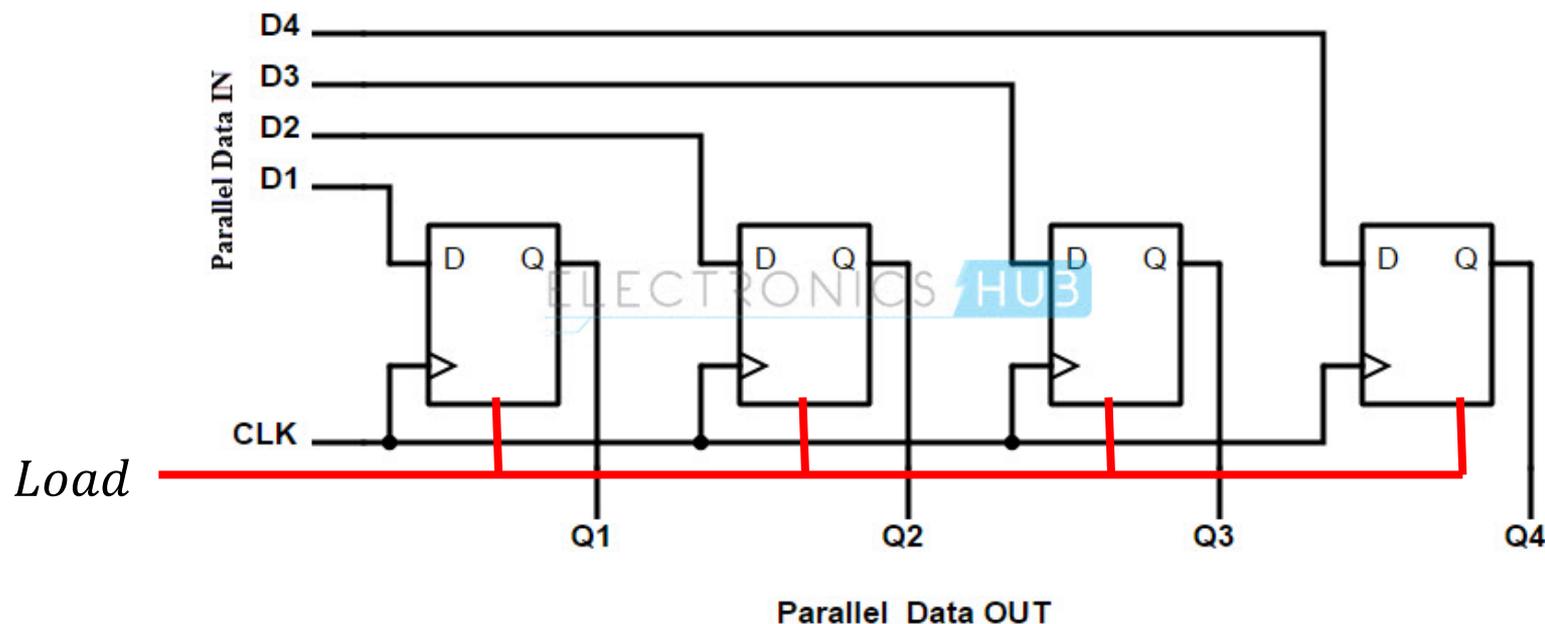


Register with Parallel Load (cont'd)

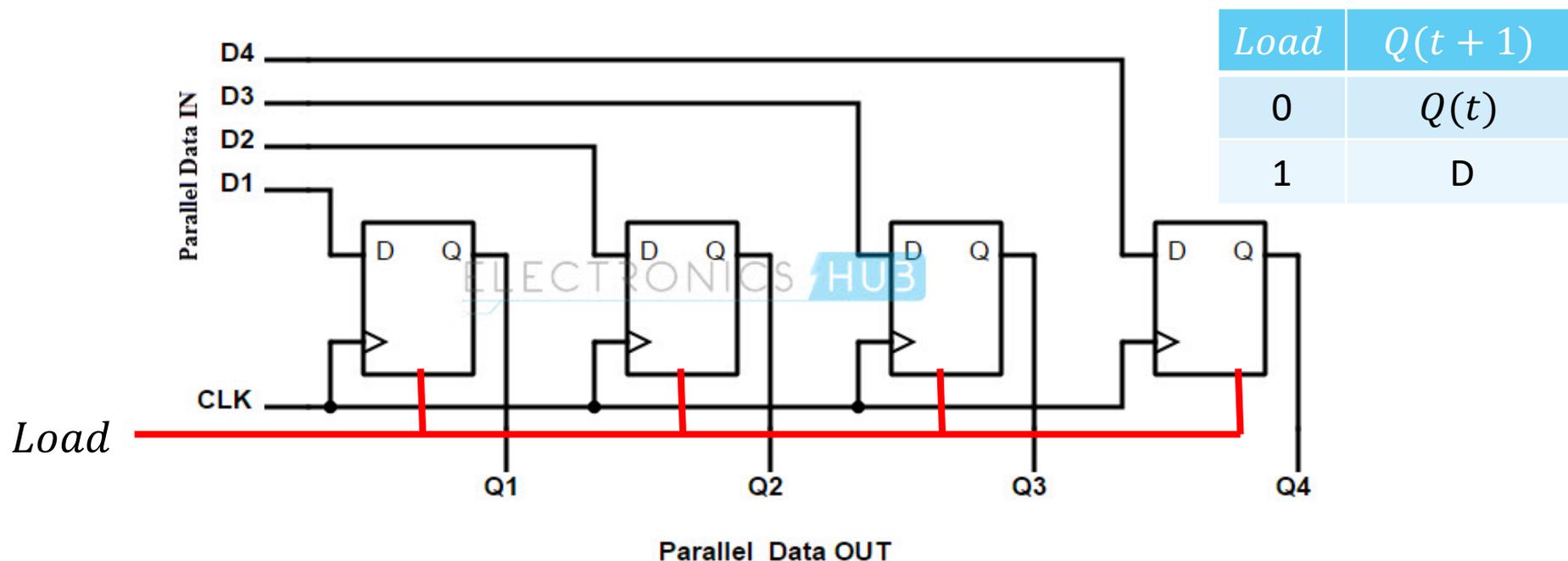- How to insert a load signal to the register with parallel load?




Register with Parallel Load (cont'd)

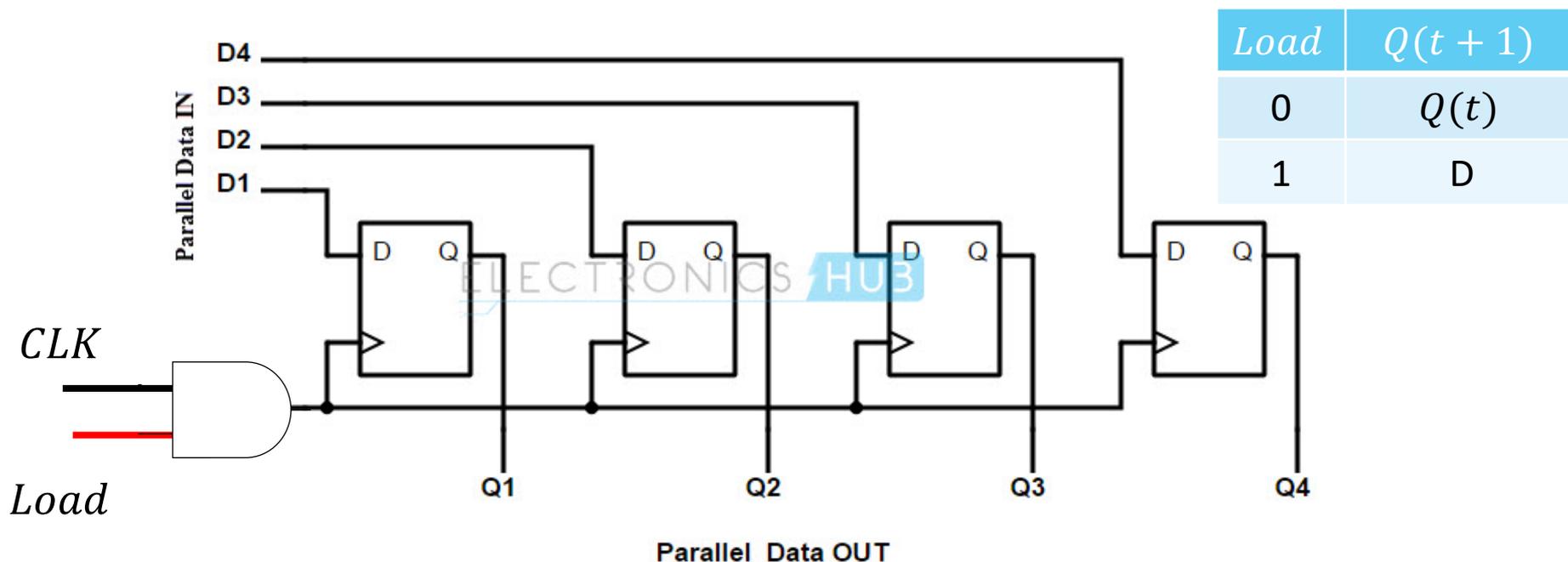- And Load and CLK signal together
- Delays the clock




Register with Parallel Load (cont'd)

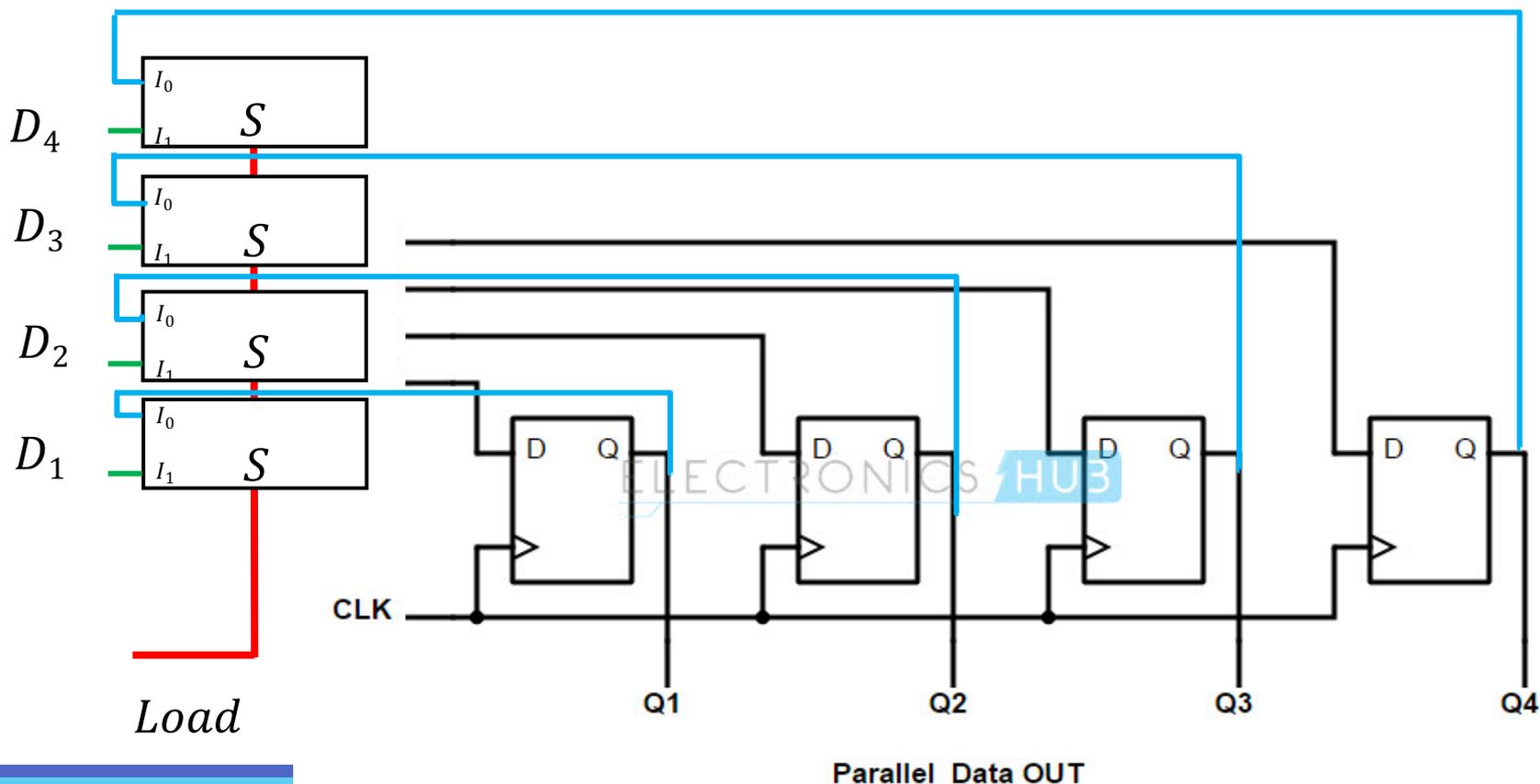- Use MUX to select the new data by load signal





Register: Sample 2

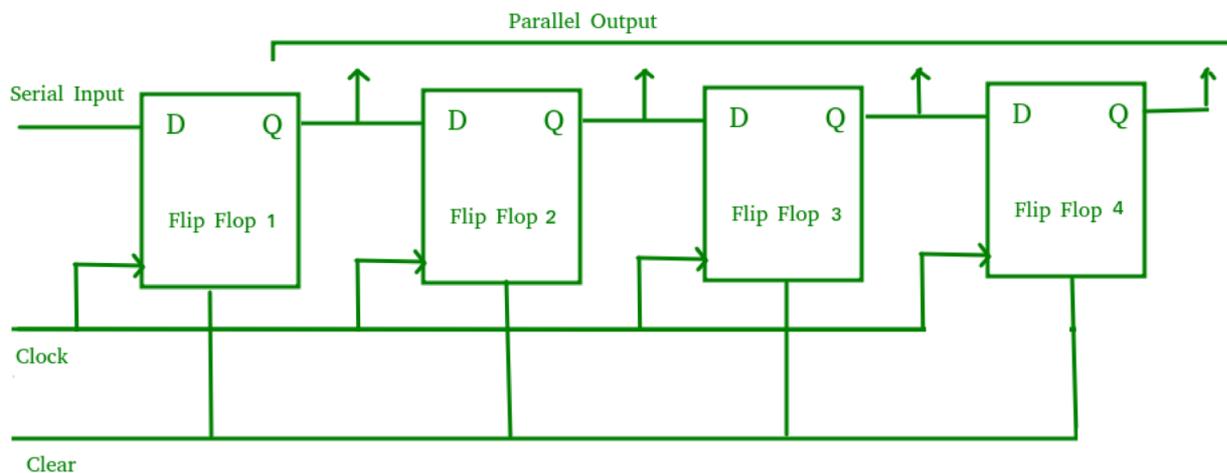- Synchronous register
- A collection of D FF




Register: Sample 1 (cont'd)

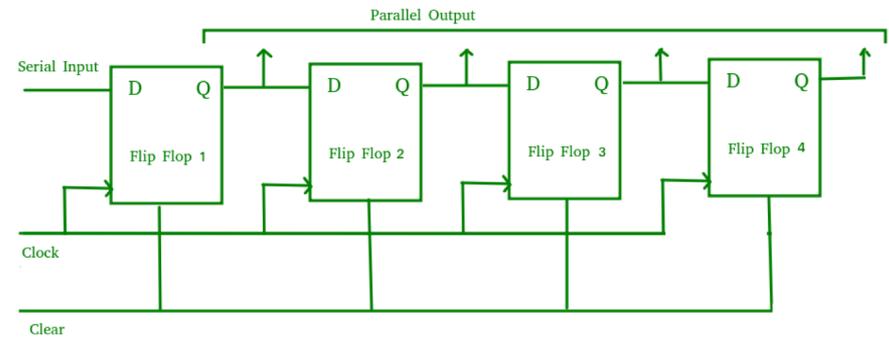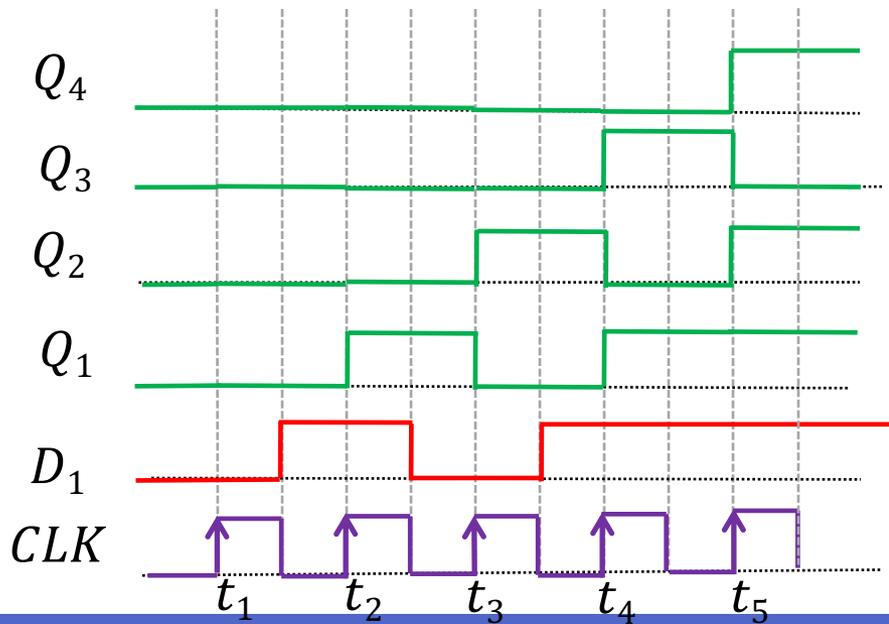




Shift Register

- 4-bit shift register

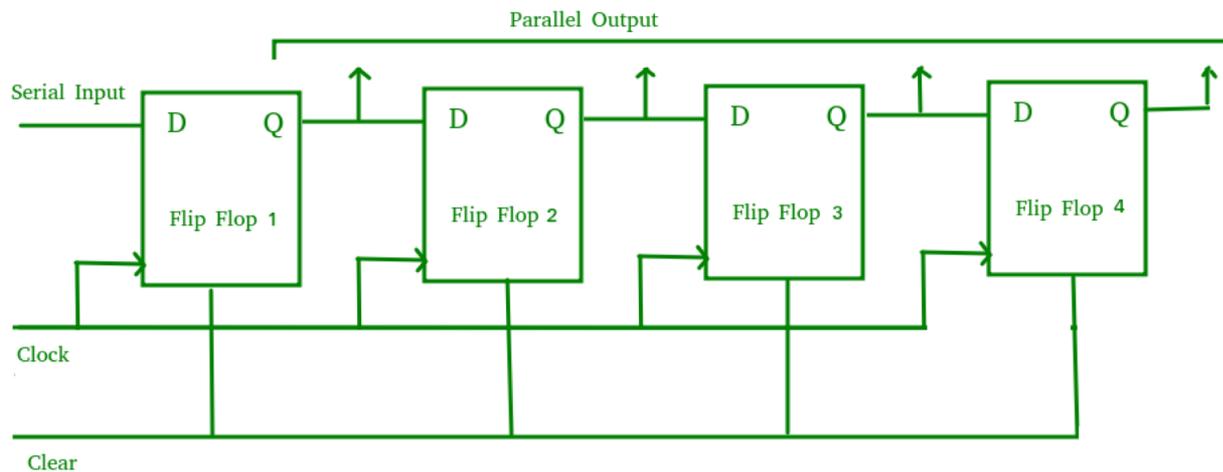


Shift Register: Types

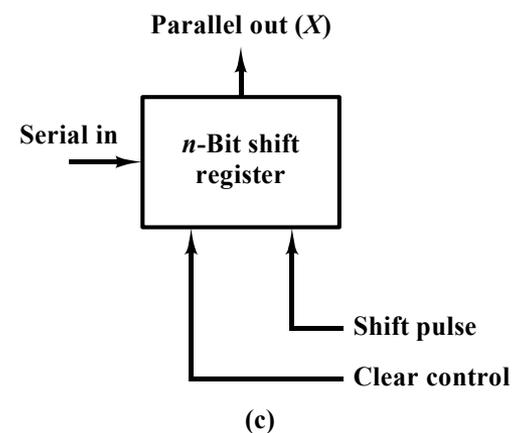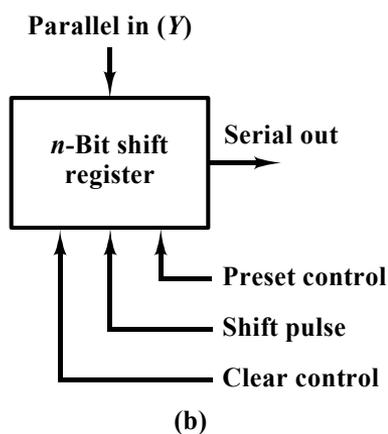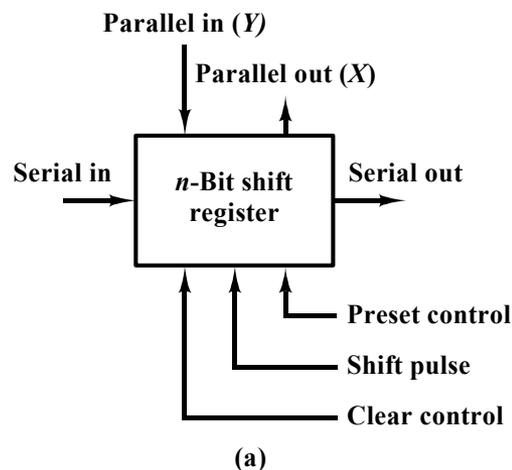- Parallel-in Parallel-out
- Serial-in Serial-out
- Serial-in Parallel-out
- Parallel-in Serial-out




Shift Register: Types (cont'd)

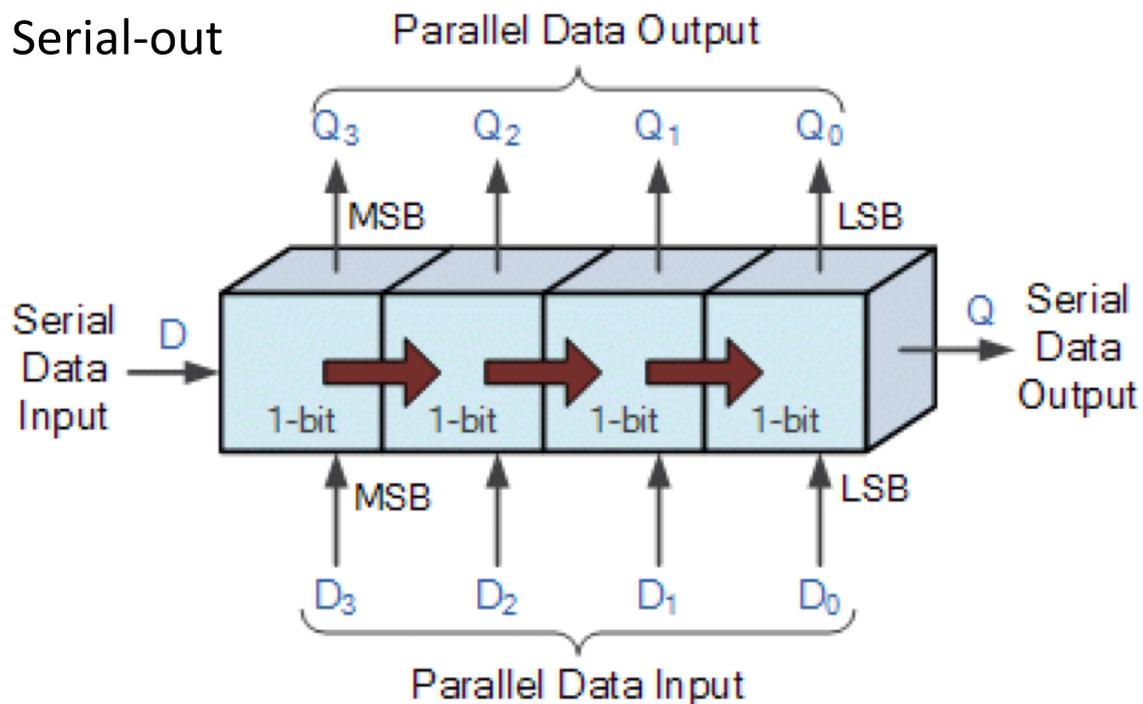- Parallel-in Parallel-out
- Serial-in Serial-out
- Serial-in Parallel-out
- Parallel-in Serial-out




Serial-in Parallel-out Shift Register

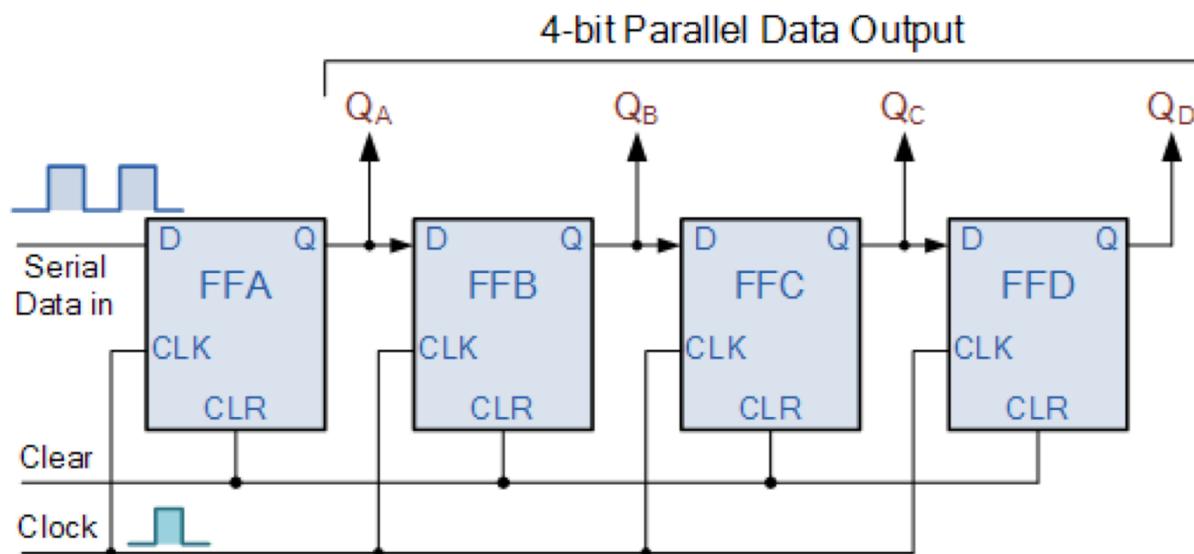- 4-bit shift register
 - Serial input
 - Parallel output




Serial-in Serial-out Shift Register

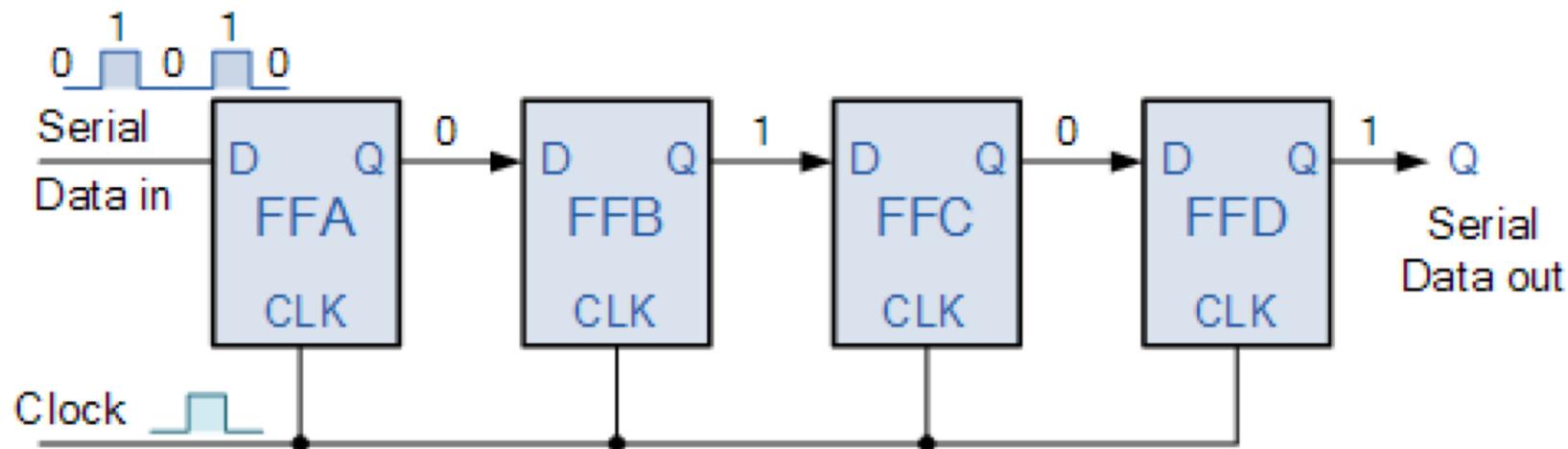- 4-bit shift register
 - Parallel input
 - Serial output




Parallel-in Parallel-out Shift Register

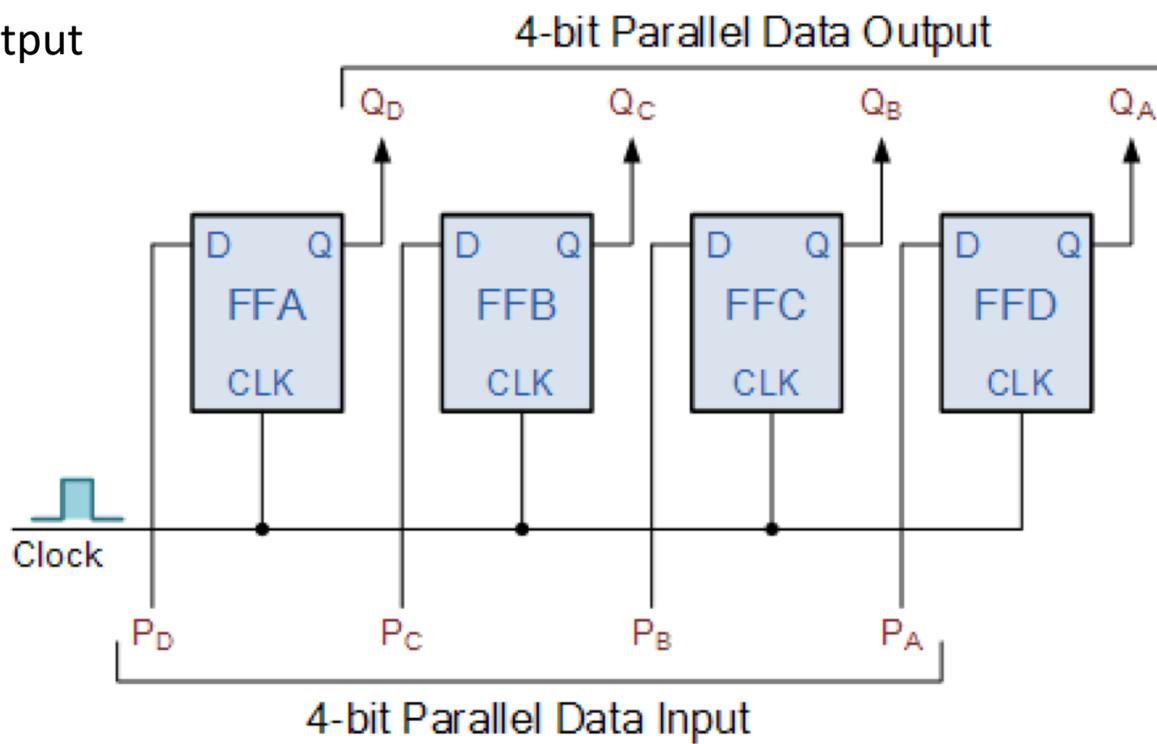- 4-bit shift register
 - Parallel input
 - Serial output




Parallel-in Serial-out Shift Register

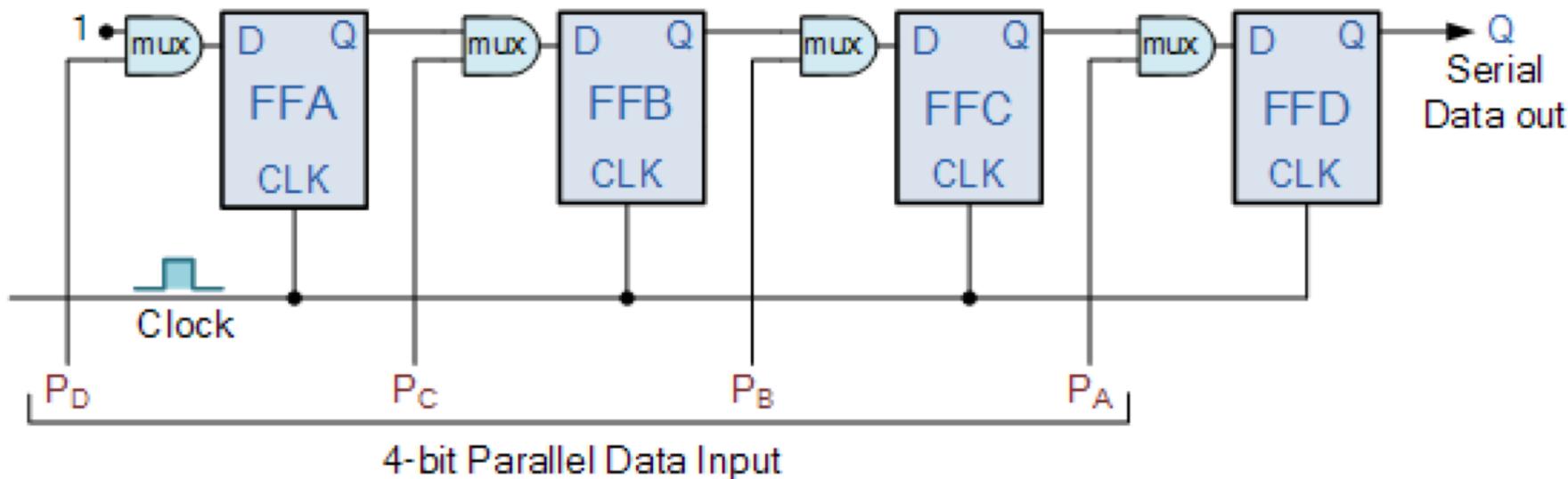- 4-bit shift register
 - Parallel input
 - Serial output




Universal Shift Register (USR)

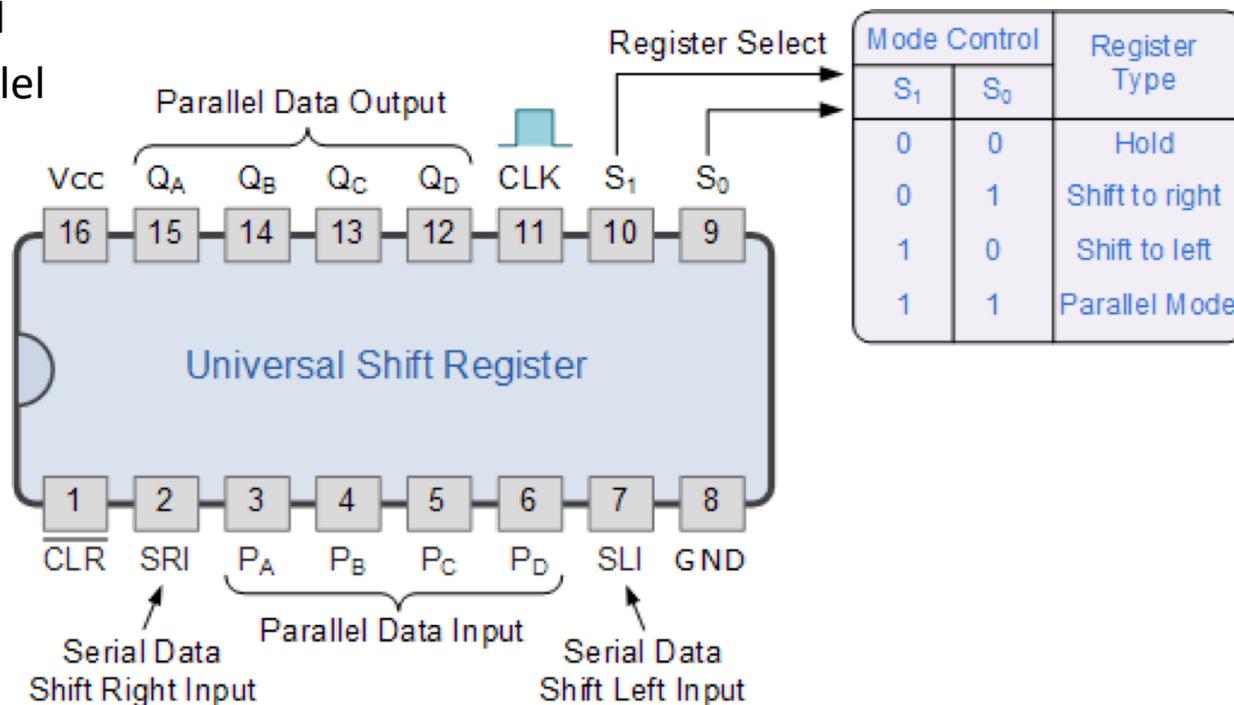- Functionalities
 - Serial-to-serial
 - Serial-to-parallel
 - Parallel-to-serial
 - Parallel-to-parallel
 - Left shifting
 - Right shifting




USR: Hold

- Hold

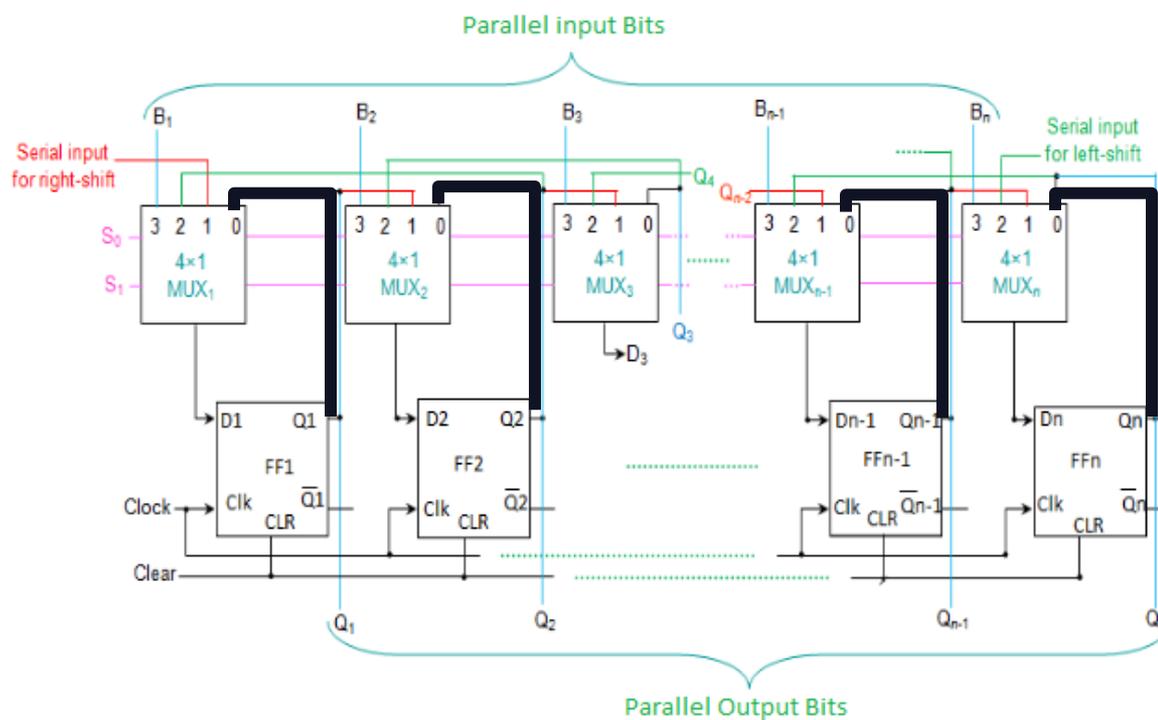


USR: Right Shift

- Right shift

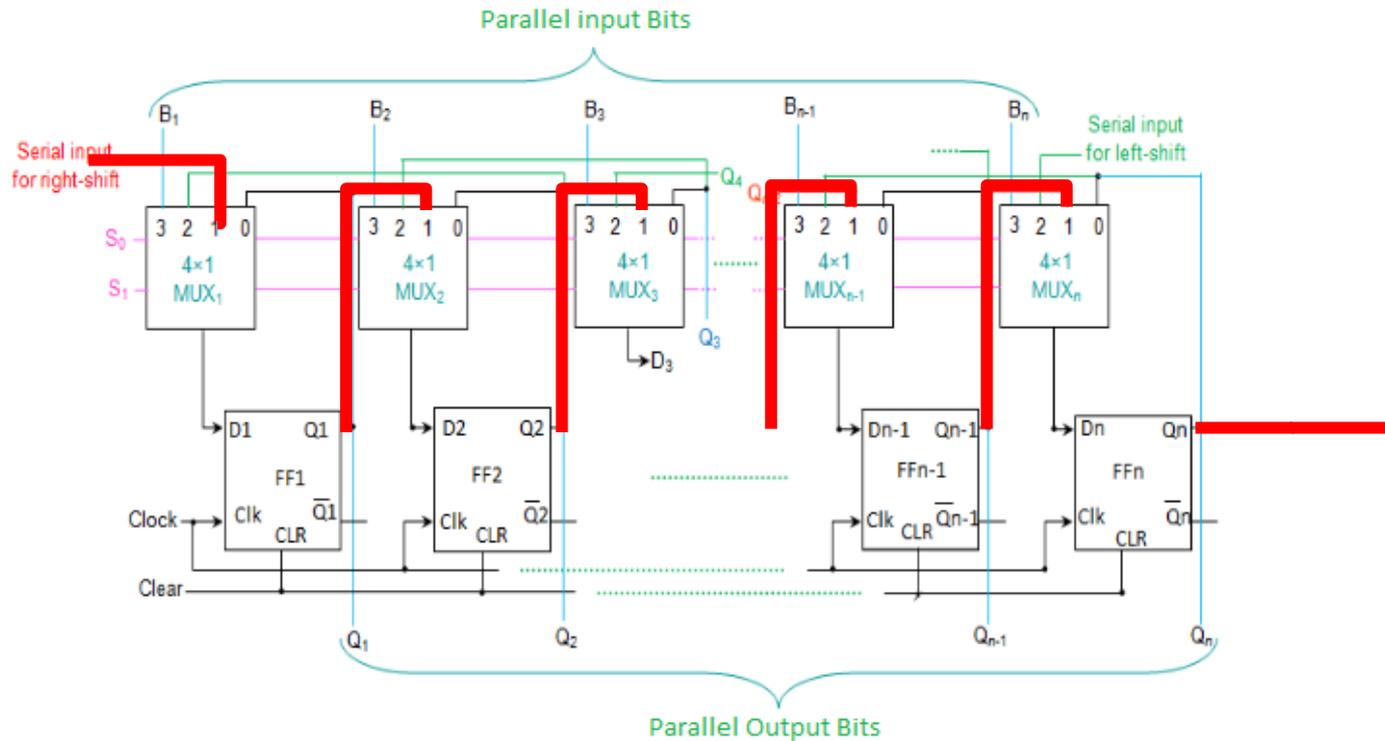


USR: Left Shift

- Left shift

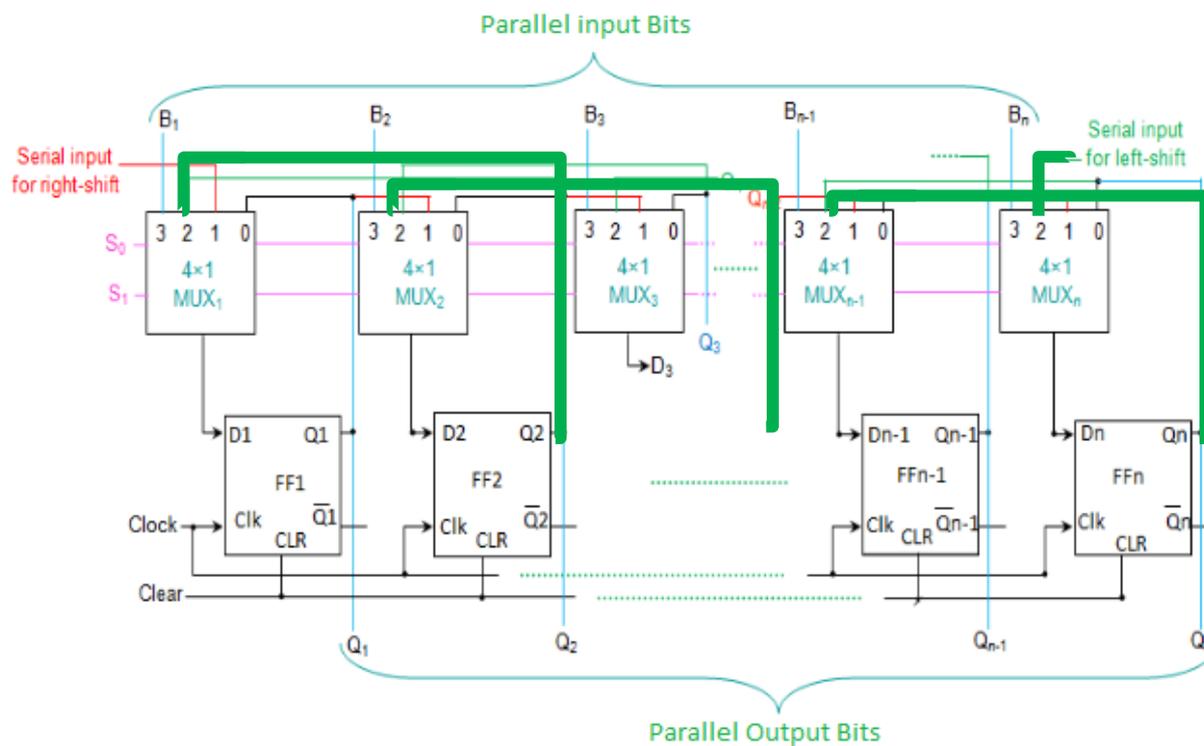


USR: Parallel Load

- Parallel Load

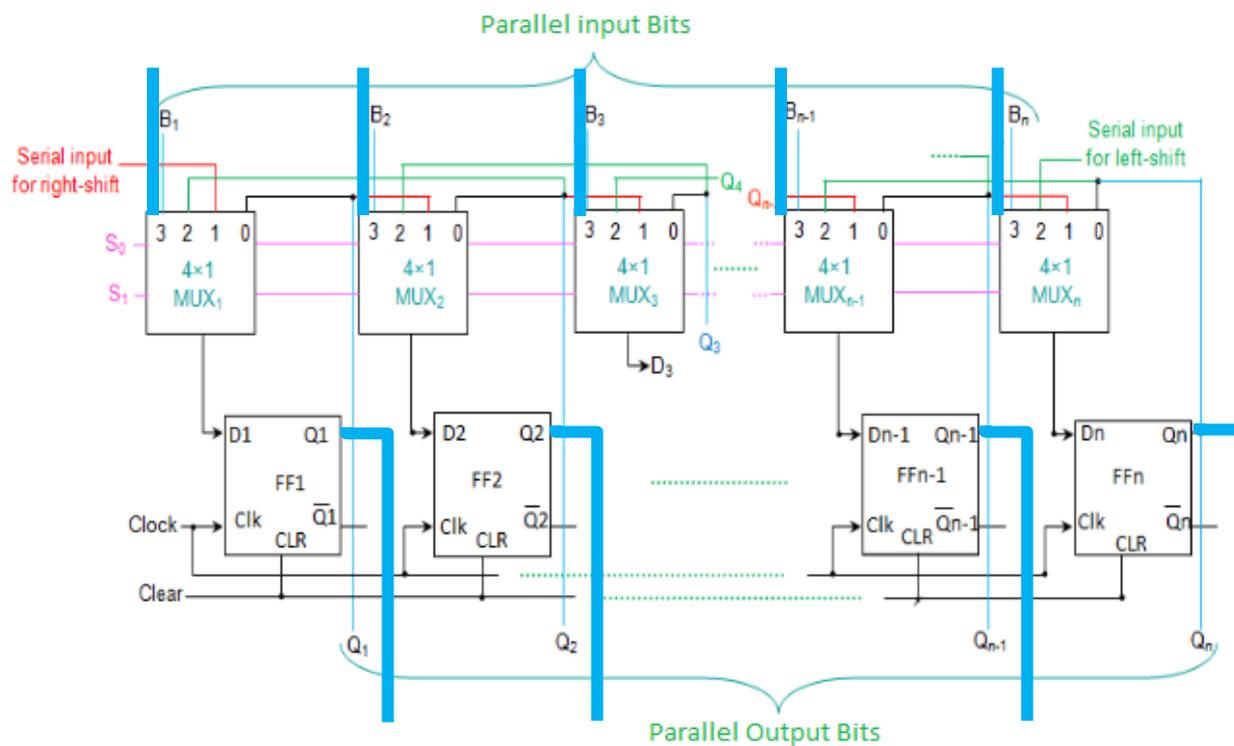


USR: All In One!

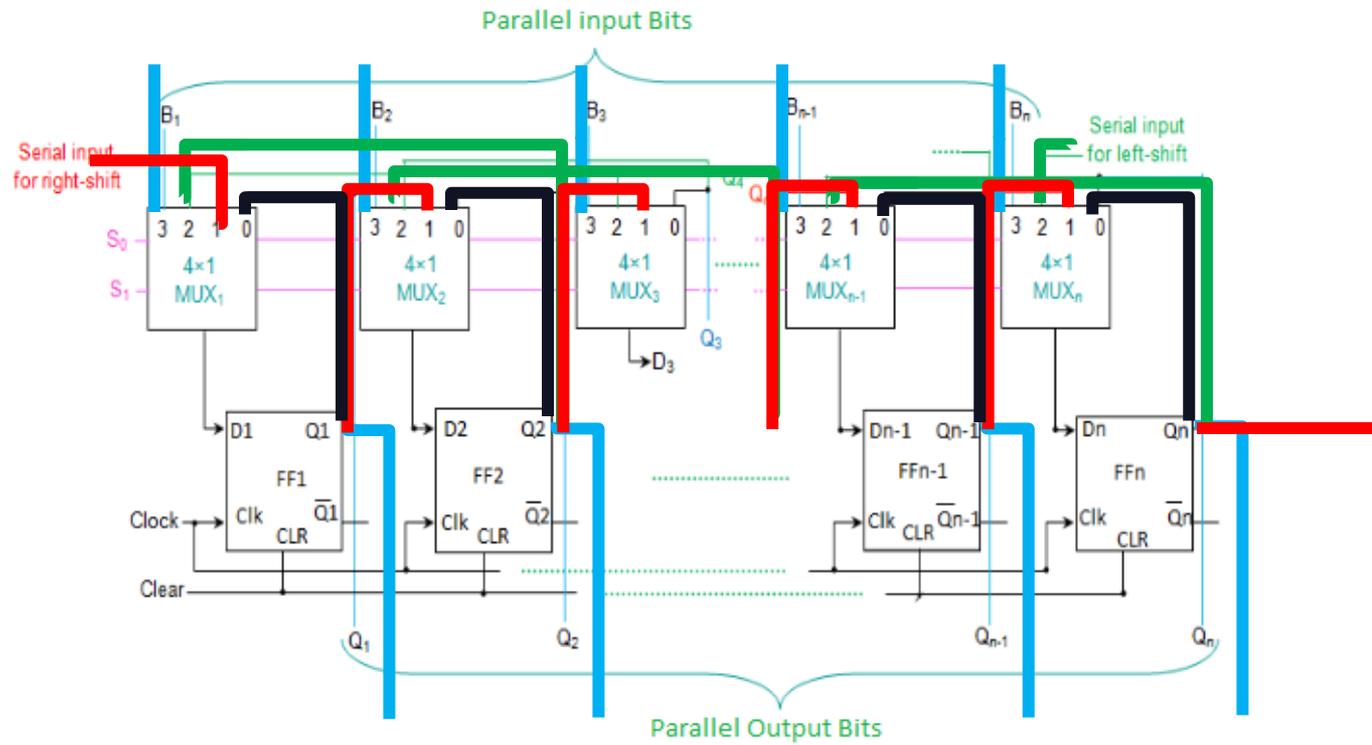- Hold
- Right shift
- Left shift
- Parallel Load



USR: All In One!!

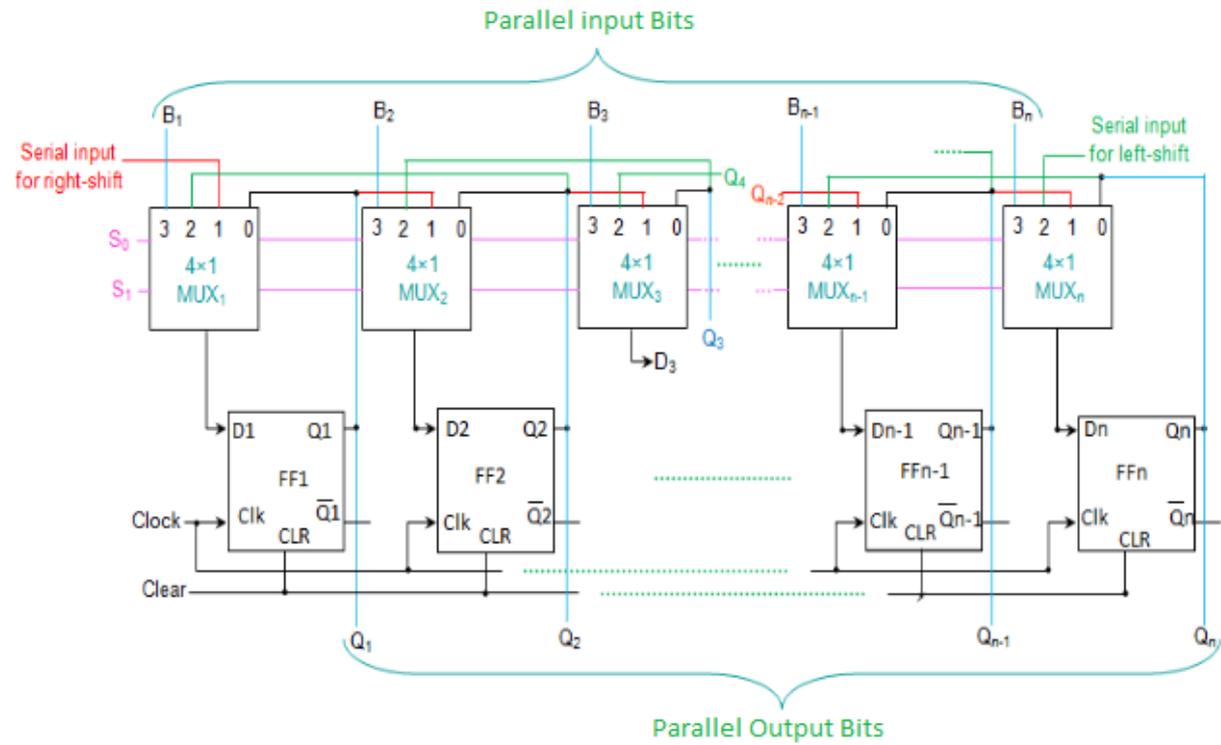- Hold
- Right shift
- Left shift
- Parallel Load



Shift Register Application


- **Send/Receive** data from computer/input device to output device /computer
- **Converting** between **serial** data and **parallel** data
 - Parallel data
 - Computers typically work with **multiple-bit** quantities
 - Serial data
 - Keyboards, mice, printers.
 - Serial port, USB, Firewire



Standard TTL Shift Registers


Device	Features
7491A	8-Bit, serial in, serial out
7496	5-Bit, serial in, serial out, asynchronous preset, parallel out, common clear
74164	8-Bit, serial in, serial out or parallel out, common clear
74165	8-Bit, serial in, serial out, asynchronous load, clock inhibit
74179	4-Bit, serial in, serial out, common clear, synchronous load, parallel out, synchronous data hold
74194	4-Bit, bidirectional, serial in, serial out, synchronous load, parallel out, clock inhibit, common clear

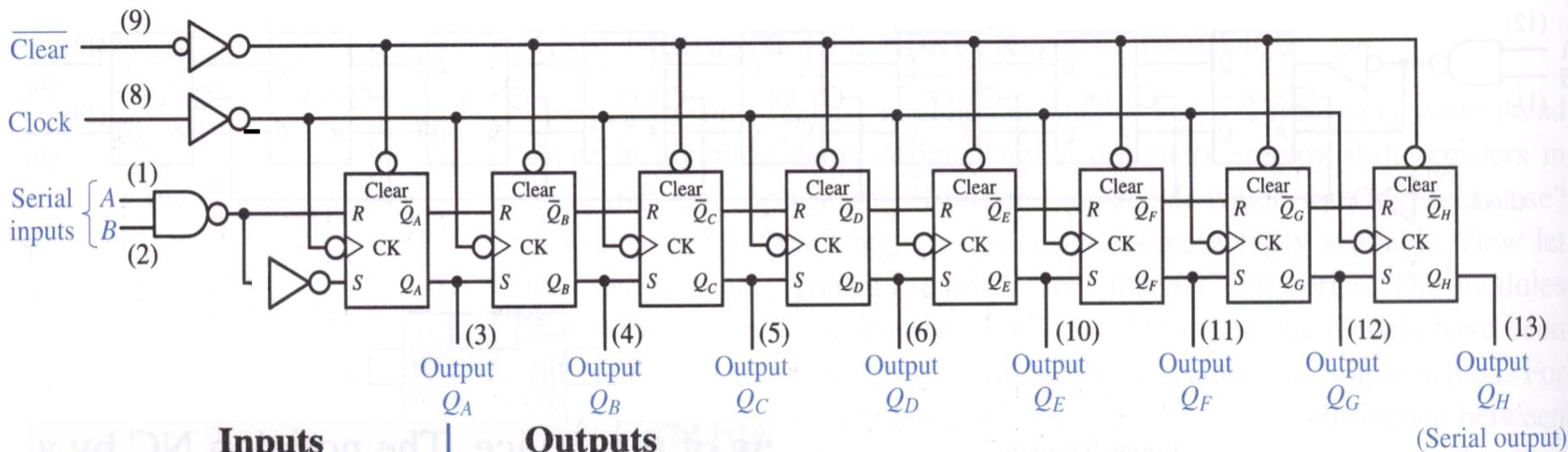74164: 8-bit, Serial In, Serial/Parallel Out



Inputs				Outputs			
$\overline{\text{Clear}}$	Clock	A	B	Q_A	Q_B	...	Q_H
L	×	×	×	L	L		L
H	L	×	×	Q_{A0}	Q_{B0}		Q_{H0}
H	↑	H	H	H	Q_{An}		Q_{Gn}
H	↑	L	×	L	Q_{An}		Q_{Gn}
H	↑	×	L	L	Q_{An}		Q_{Gn}

74164 operation

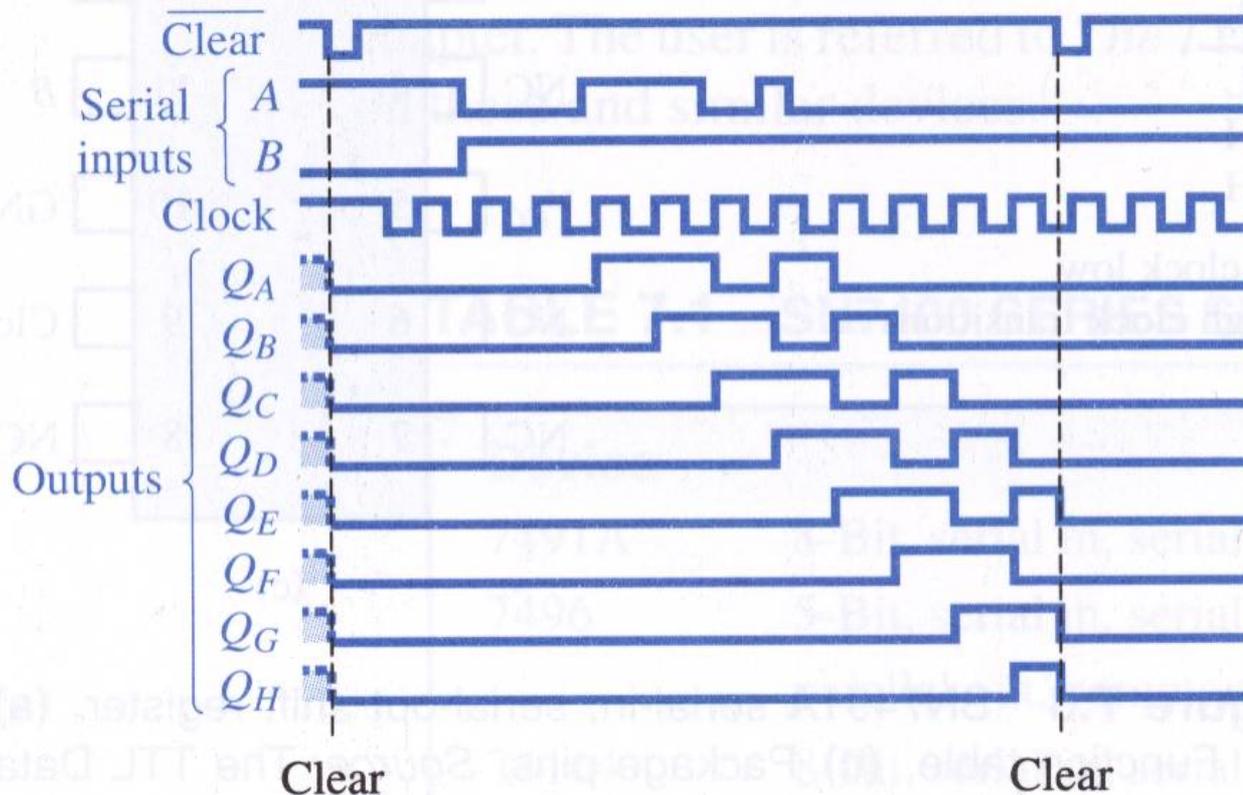

74194: 4-bit, Serial In, Serial/Parallel out

- 74194: 4-bit, bidirectional, serial-in, serial/parallel out shift register
 - Asynchronous common clear
 - Synchronous load

Inputs				Internal signals ($i = A, B, C, D$)	Mode
Clear	S_0	S_1	Clock	S_i	
L	×	×	×	×	Asynchronous clear
H	L	L	×	×	Clock inhibit (data hold)
H	L	H	↑	Q_{i+1}	Shift left
H	H	L	↑	Q_{i-1}	Shift right
H	H	H	↑	i	Parallel load

74194 operation


Internal clock $CK = CLOCK + S0' \cdot S1'$

- When $S0$ and $S1$ are both 0, $CK = 1$; hold

Set input of internal FF (e.g. B) is

$$S_B = Q_C \cdot S0' + Q_A \cdot S1' + B \cdot S0 \cdot S1$$

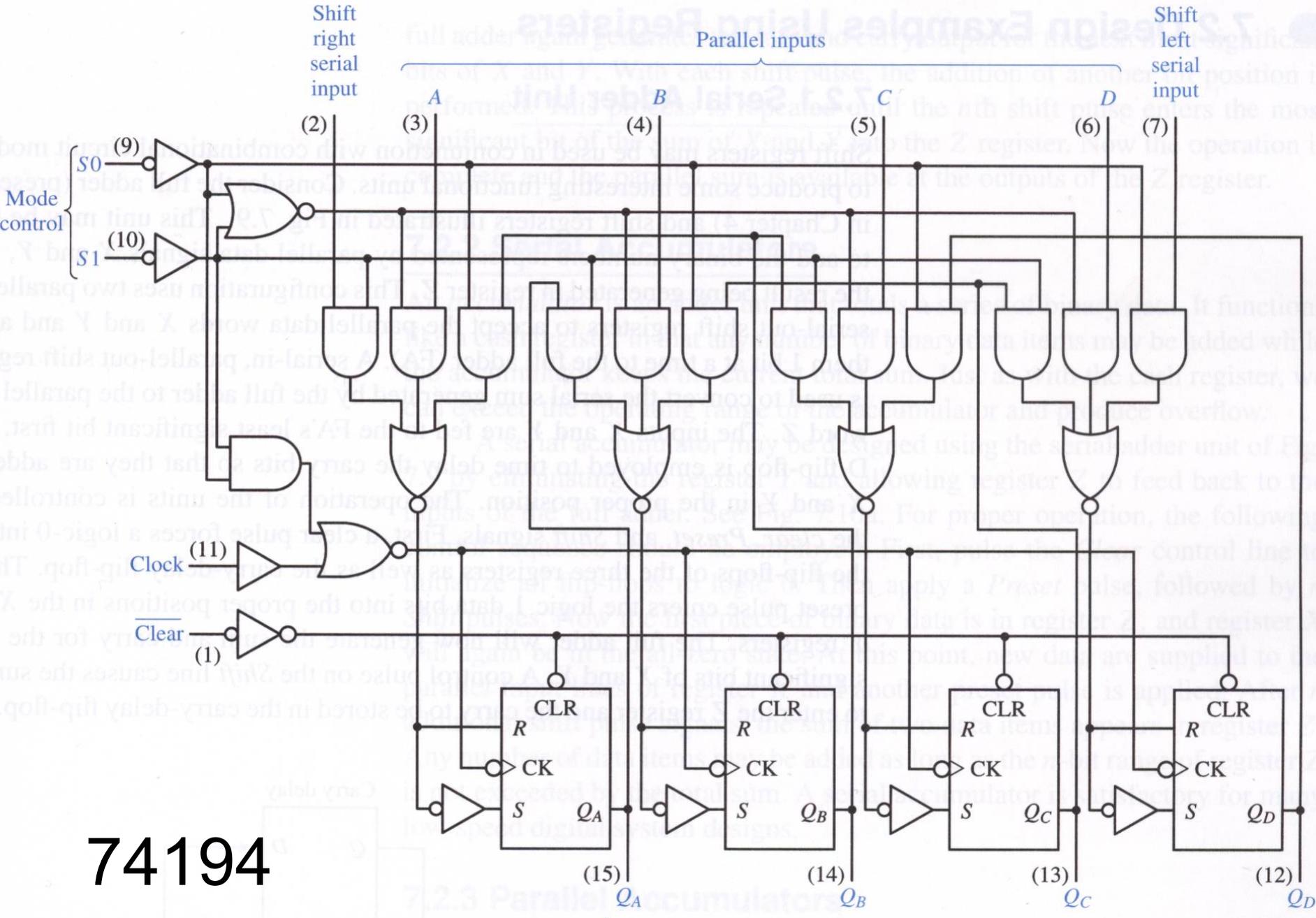- $S1=1$ & $S0=0 \Rightarrow S_B = Q_C$; shift left
- $S1=0$ & $S0=1 \Rightarrow S_B = Q_A$; shift right
- $S1=1$ & $S0=1 \Rightarrow S_B = B$; external load
- Synchronous parallel load



74194

Thank You

